

D 12394

(Pages : 2)

Name.....

Reg. No.....

**THIRD SEMESTER B.Sc. DEGREE EXAMINATION, NOVEMBER 2016**

(CUCBCSS—UG)

Computer Science

**BCS 3B 04—FUNDAMENTALS OF DIGITAL ELECTRONICS**

Time : Three Hours

Maximum : 80 Marks

**Part A**

*Answer all the questions.*

*Each question carries 1 mark.*

1. What is nibble ?
2. Define base of a number system.
3. What is the Gray code for the decimal number 6 ?
4. How many AND gates are required to realize  $Y = CD + EF + G$ .
5. For JK flip-flop with  $J = 1$  and  $K = 0$ , the output after clock pulse will be \_\_\_\_\_?
6. On K map grouping of 0's produces \_\_\_\_\_ expression.
7. A device which convert BCD to seven segment is \_\_\_\_\_.
8. How many select lines will a 16 to 1 multiplexer will have ?
9. A full adder is characterized by \_\_\_\_\_ inputs and \_\_\_\_\_ outputs.
10. How many address bits are required to represent a 32 K memory ?

(10 × 1 = 10 marks)

**Part B**

*Answer all the questions.*

*Each question carries 2 marks.*

11. Design an exclusive OR gate with three inputs.
12. What are synchronous counters ?
13. What are excess-3 codes ?
14. What is a shift register ? Can a shift register be used as a counter ?
15. Prove that  $xy + xz' + yz = xy + x'z$ .

(5 × 2 = 10 marks)

Turn over

**Part C**

Answer any **five** questions.  
Each question carries 4 marks.

16. Convert  $(25.16)_8$  to binary and  $(946.152)_{16}$  to binary.
17. Perform BCD addition on (a)  $67 + 53$  ; (b)  $55 + 25$ .
18. State and prove De Morgans theorems.
19. What is a half adder ? Explain a half adder with truth table and logic diagram.
20. What is a decoder ? Compare a decoder and a demultiplexer with suitable block diagrams.
21. With the help of a truth table explain the working of an  $8 \times 3$  encoder. Draw the logic diagram using gates.
22. What is a flip-flop ? What is the difference between a latch and a flip-flop ? List out the applications of flip-flop.
23. Prove that any Boolean function can be expressed as the product of max terms or sums.

(5 × 4 = 20 marks)

**Part D**

Answer any **five** questions.  
Each question carries 8 marks.

24. Using K-map simplify the expression  $f(w, x, y, z) = \Sigma (1, 3, 7, 11, 15)$  and  $d(w, x, y, z) = \Sigma (0, 2, 5)$ . Draw the logic diagram of the simplified expression.
25. Explain the following conversions with suitable examples : (a) decimal to Octal ; (b) Octal to binary ; (c) Hexadecimal to Octal.
26. With the help of a neat diagram explain the working of successive approximation A/D converter .
27. Distinguish between combinational logic circuits and sequential logic circuits. How are the design requirements of combinational circuits specified ?
28. Design a 3 bit up/down counter using JK flip-flop and explain its function with timing diagram.
29. Simplify the Boolean expression  $F = (A + E + C)(A + B + C)(A + E)$ . Realize the simplified expression using only NAND gates.
30. Explain the operation of Master slave JK flip-flop with truth table and logic diagram.
31. Write notes on :
  - (a) Basic logic gates.
  - (b) Demultiplexer trees.
  - (c) Simultaneous method of A/D conversion.

(5 × 8 = 40 marks)